

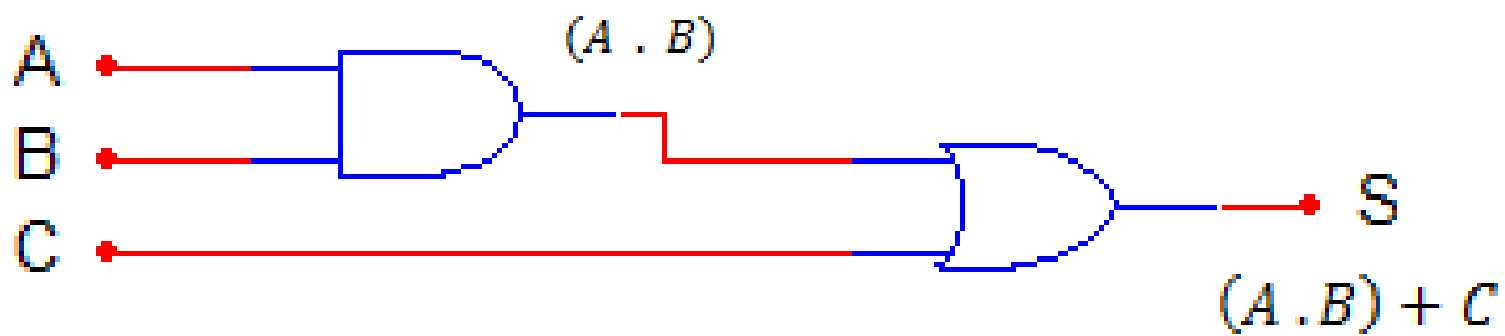



SISTEMAS DIGITAIS

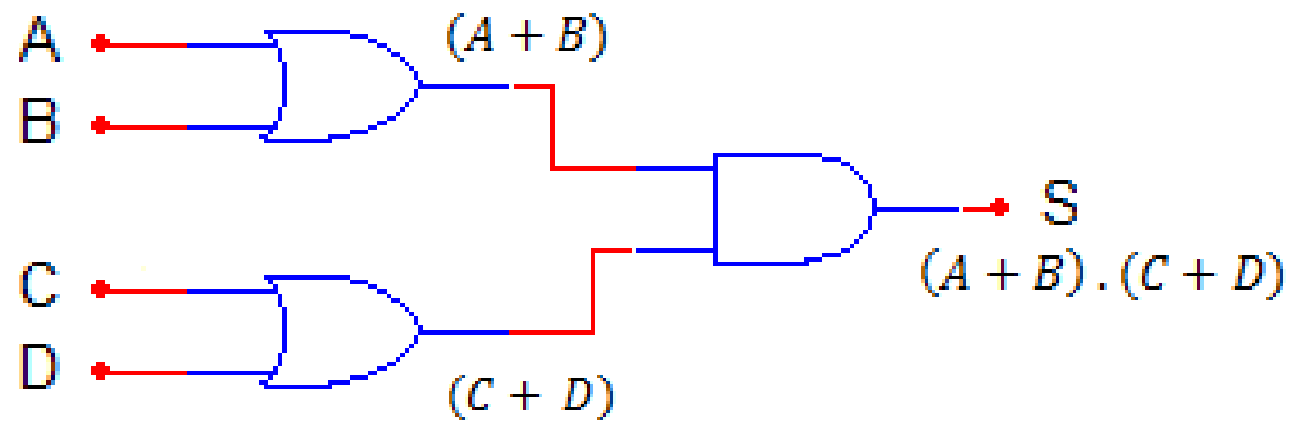
EXPRESSÕES BOOLEANAS GERADAS POR CIRCUITOS LÓGICOS



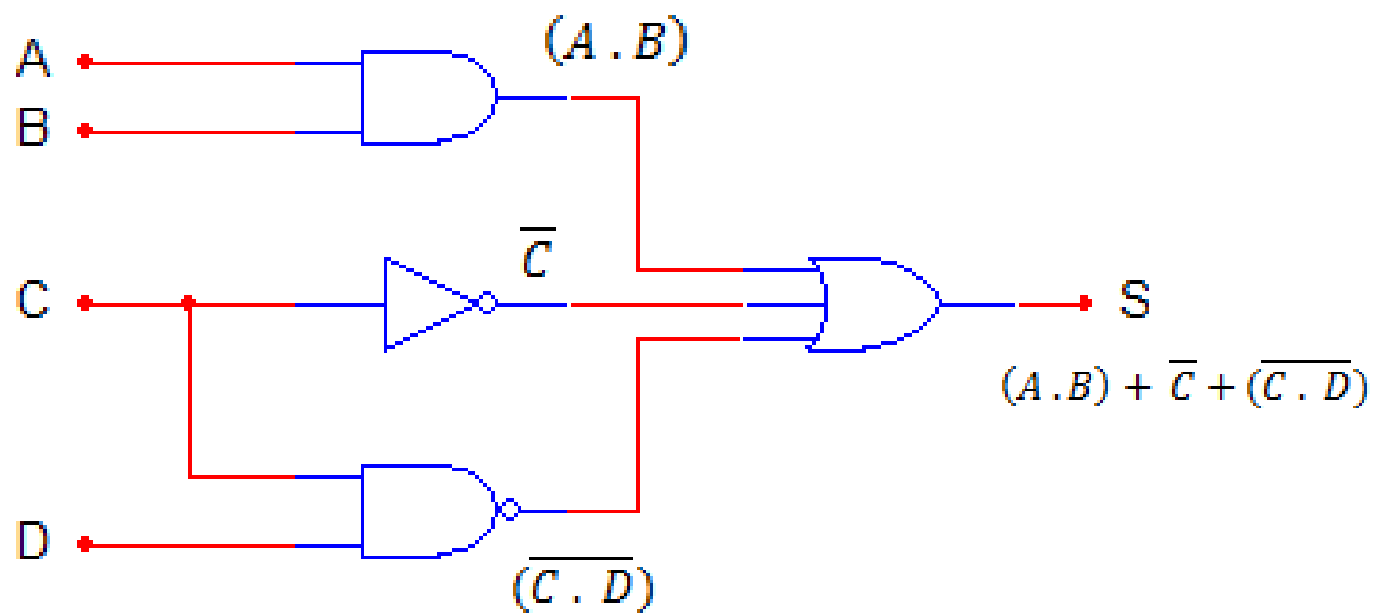



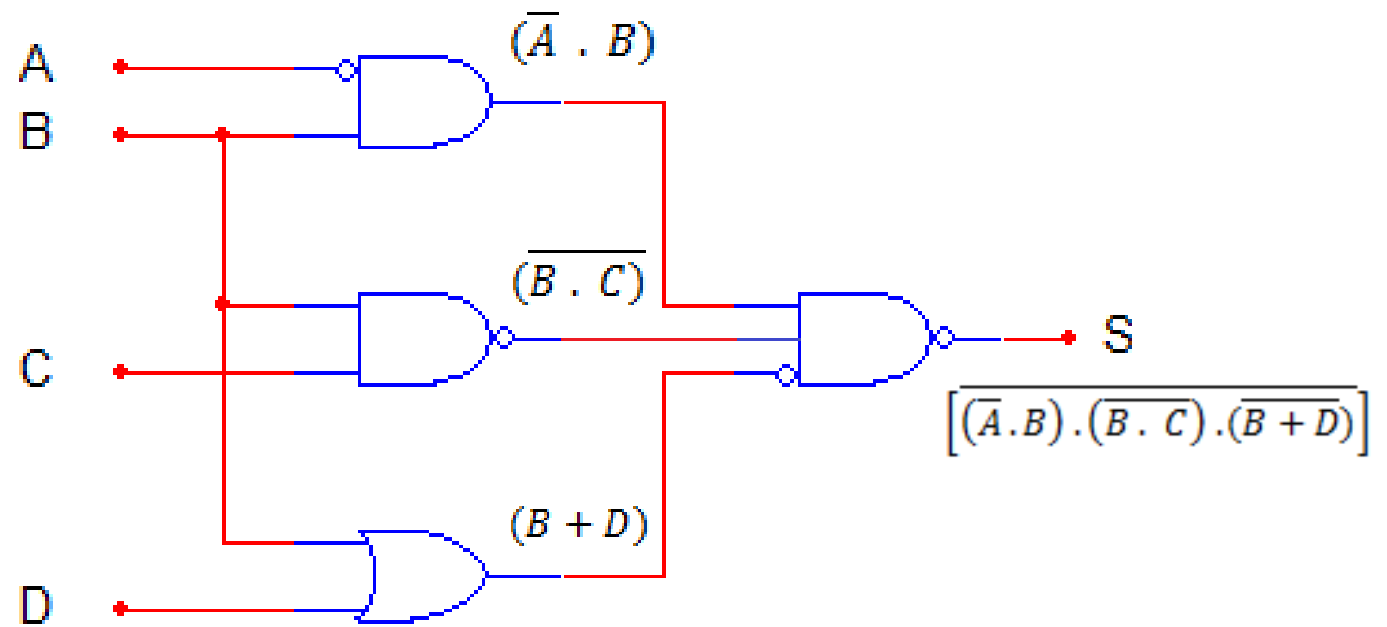



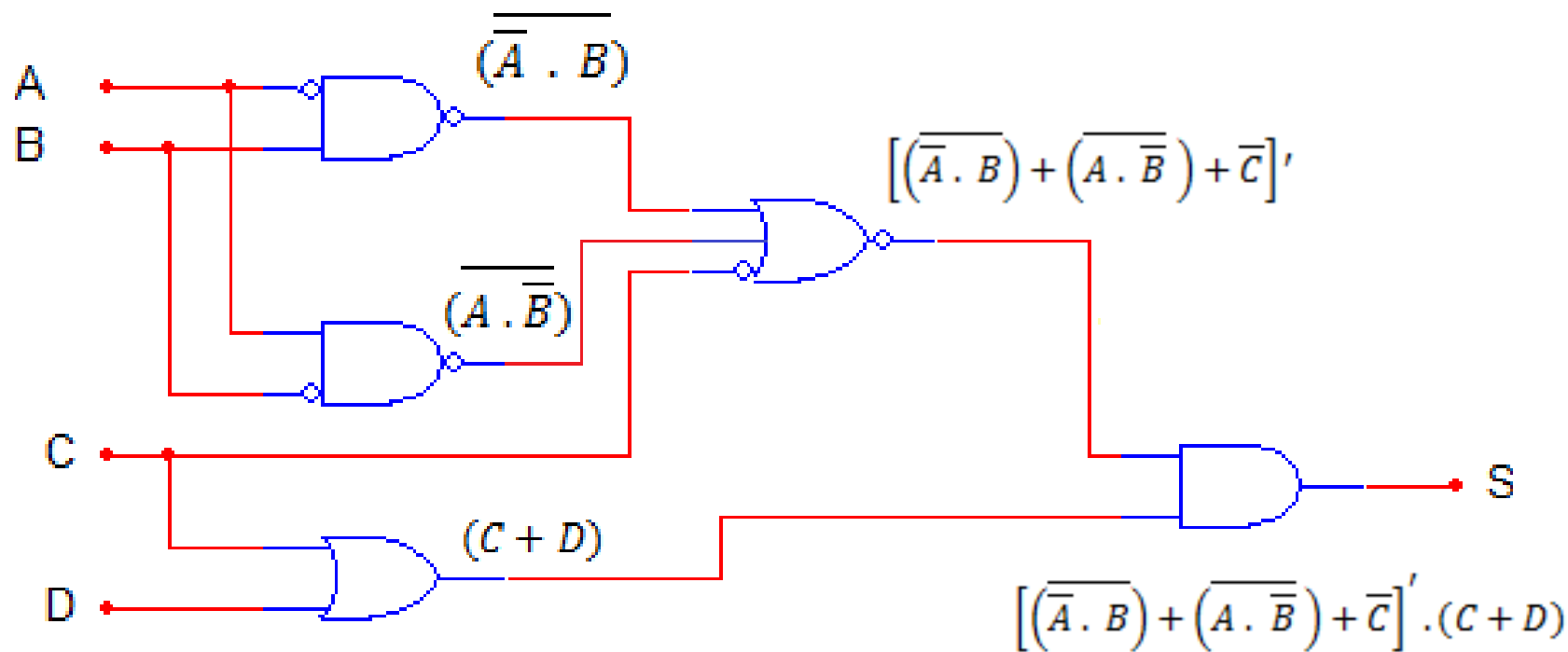


CIRCUITOS OBTIDOS DE EXPRESSÕES BOOLEANAS


$$S = (A + B) \cdot C \cdot (B + D)$$

① $(A + B)$




② $(B + D)$

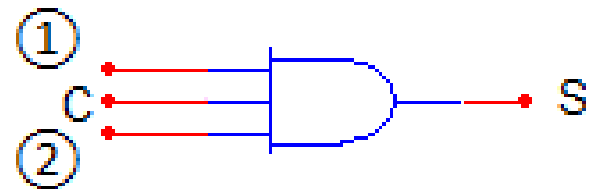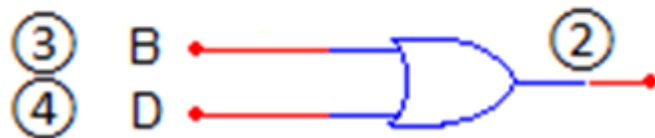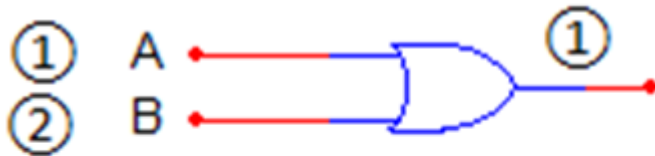


$$S = (A + B) \cdot C \cdot (B + D)$$

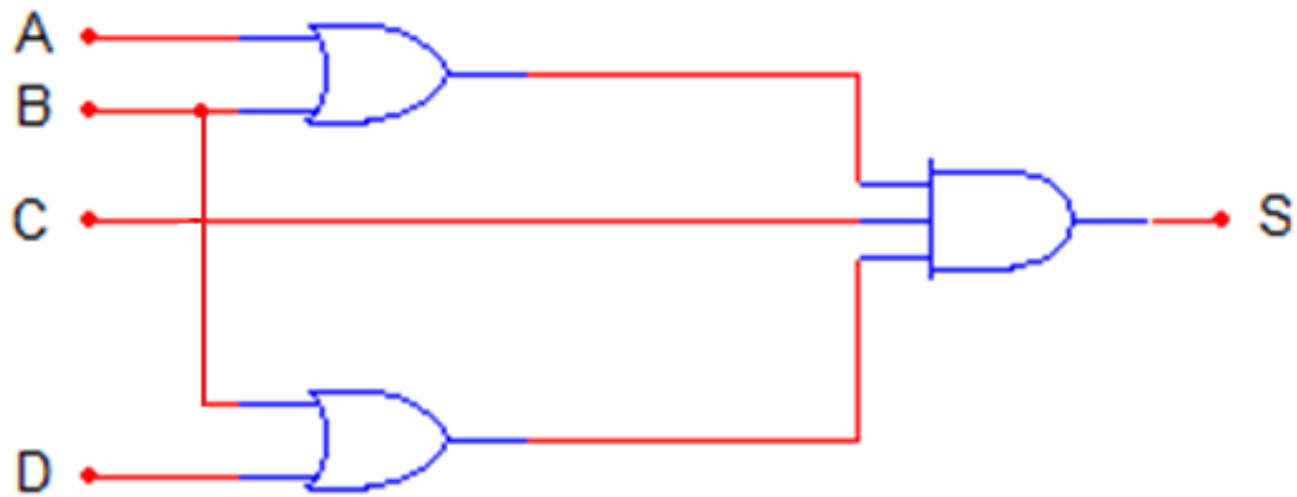



$$S = A . B . C + (A + B) . C$$

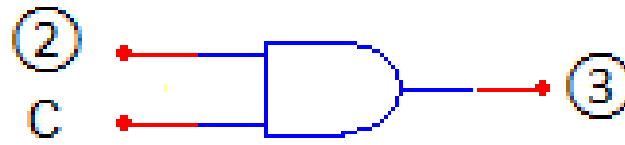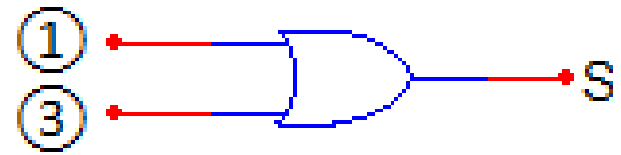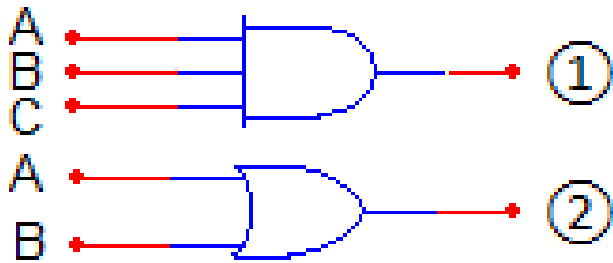
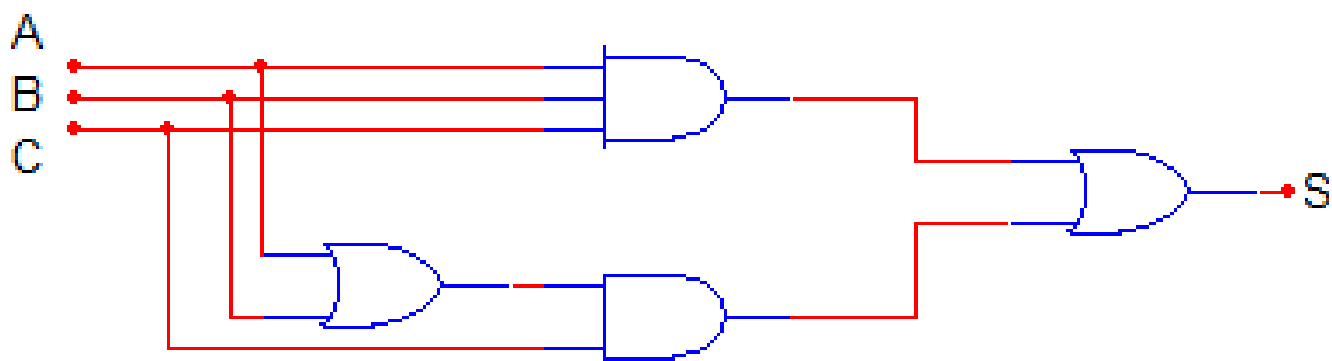
$$S = A \cdot B \cdot C + (A + B) \cdot C$$


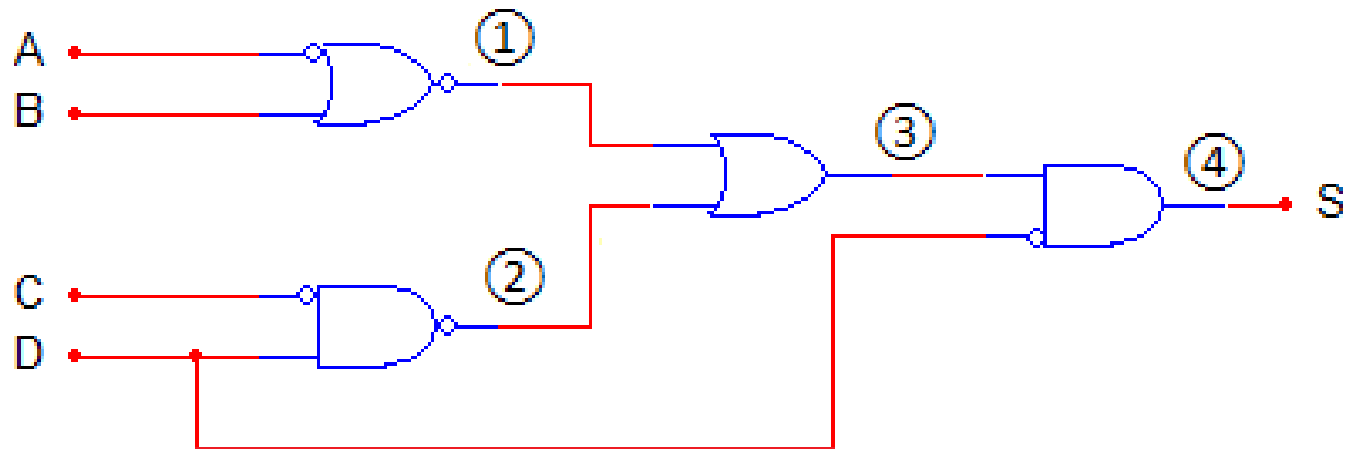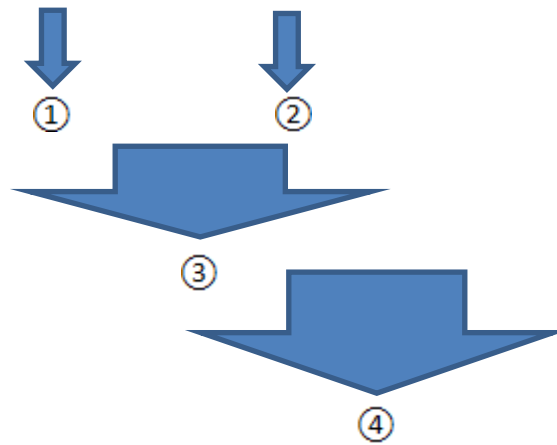
$$S = [(\overline{A + B}) + (\overline{C \cdot D})] \cdot \overline{D}$$



$$S = \left[(\overline{A} \cdot B) + (\overline{C} \cdot \overline{D}) \right]' \cdot E + [(A \cdot \overline{D} \cdot \overline{E}) + (C \cdot D \cdot E)] \cdot \overline{A}$$

